



NAME OF THE EXAMINATION: II B.TECH II SEM REGULAR (R-20)

BRANCH: ECE - 'A & B' SECTION

NAME OF THE SUBJECT: DICD

1.Priority encoder 3-8 vhdl code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity priorityencoder3_8 is
port( clk : in std_logic;
din : in std_logic_vector( 7 downto 0);
yout : out std_logic_vector( 2 downto 0));
end priorityencoder3_8;

architecture Behavioral of priorityencoder3_8 is

begin
process (din,clk)
begin

if (clk'event and clk ='1' and din(7) ='1') then yout <= "000";
elsif (clk'event and clk ='1' and din(6) ='1') then yout <= "001";
elsif (clk'event and clk ='1' and din(5) ='1') then yout <= "010";
elsif (clk'event and clk ='1' and din(4) ='1') then yout <= "011";
elsif (clk'event and clk ='1' and din(3) ='1') then yout <= "100";
elsif (clk'event and clk ='1' and din(2) ='1') then yout <= "101";
elsif (clk'event and clk ='1' and din(1) ='1') then yout <= "110";
elsif (clk'event and clk ='1' and din(0) ='1') then yout <= "111";

end if;
end process;
end Behavioral;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```



SRI VASAVI INSTITUTE OF ENGINEERING & TECHNOLOGY

Accredited by NAAC 'A' Grade & NBA

(Approved by AICTE, New Delhi & Affiliated to JNTU Kakinada),
(An ISO 9001:2015 Certified Institute)

Nandamuru, Pedana Mandal – 521 369



```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

entity pririty_encoder_tb is

```
-- Port ( );
end pririty_encoder_tb;
```

architecture Behavioral of pririty_encoder_tb is

component priorityencoder3_8 is

```
port( clk : in std_logic;
din : in std_logic_vector( 7 downto 0);
yout : out std_logic_vector( 2 downto 0));
end component;
```

```
signal clk : std_logic;
signal din : std_logic_vector(7 downto 0):="00000000";
signal yout : std_logic_vector(2 downto 0);
begin
```

```
p1:priorityencoder3_8 port map (clk => clk,din(0) => din(0) ,din(1) => din(1) ,din(2) => din(2)
,din(3) => din(3) ,din(4) => din(4) ,din(5) => din(5) ,din(6) => din(6),din(7) => din(7) ,yout(0)
=> yout(0),yout(1) => yout(1),yout(2) => yout(2));
```

process

begin

clk <= '0'; wait for 5 ns;

clk <= '1'; wait for 5 ns;

end process;

process

begin

din(7) <= '1'; wait for 10 ns;

din(7) <= '0'; wait for 80 ns;

end process;

process

begin

din(6) <= '1'; wait for 20 ns;

din(6) <= '0'; wait for 80 ns;

end process;

process

begin

din(5) <= '1'; wait for 30 ns;



SRI VASAVI INSTITUTE OF ENGINEERING & TECHNOLOGY

Accredited by NAAC 'A' Grade & NBA

(Approved by AICTE, New Delhi & Affiliated to JNTU Kakinada),
(An ISO 9001:2015 Certified Institute)


Nandamuru, Pedana Mandal – 521 369



```

din(5) <= '0'; wait for 80 ns;
end process;
process
begin
din(4) <= '1'; wait for 40 ns;
din(4) <= '0'; wait for 80 ns;
end process;
process
begin
din(3) <= '1'; wait for 50 ns;
din(3) <= '0'; wait for 80 ns;
end process;
process
begin
din(2) <= '1'; wait for 60 ns;
din(2) <= '0'; wait for 80 ns;
end process;
process
begin
din(1) <= '1'; wait for 70 ns;
din(1) <= '0'; wait for 80 ns;
end process;
process
begin
din(0) <= '1'; wait for 80 ns;
din(0) <= '0'; wait for 80 ns;
end process;

end Behavioral;
```

 

2. Verilog source code to realize ALU.

```
module alu(
    input [7:0] A, B,      // 8-bit inputs
    input [3:0] ALU_Sel,  // 4-bit ALU control signal
    output reg [7:0] ALU_Out, // 8-bit output
    output CarryOut       // Carry-out flag
);
    wire [8:0] tmp;
    assign tmp = {1'b0, A} + {1'b0, B};
    assign CarryOut = tmp[8]; // Carry-out flag

    always @(*) begin
        case(ALU_Sel)
            4'b0000: ALU_Out = A + B;      // Addition
            4'b0001: ALU_Out = A - B;      // Subtraction
```

```

4'b0010: ALU_Out = A * B;      // Multiplication
4'b0011: ALU_Out = A / B;      // Division
4'b0100: ALU_Out = A << 1;     // Logical shift left
4'b0101: ALU_Out = A >> 1;     // Logical shift right
4'b0110: ALU_Out = {A[6:0], A[7]}; // Rotate left
4'b0111: ALU_Out = {A[0], A[7:1]}; // Rotate right
4'b1000: ALU_Out = A & B;      // Bitwise AND
4'b1001: ALU_Out = A | B;      // Bitwise OR
4'b1010: ALU_Out = A ^ B;      // Bitwise XOR
4'b1011: ALU_Out = ~(A | B);   // Bitwise NOR
4'b1100: ALU_Out = ~(A & B);   // Bitwise NAND
4'b1101: ALU_Out = ~(A ^ B);   // Bitwise XNOR
4'b1110: ALU_Out = (A > B) ? 8'd1 : 8'd0; // A > B comparison
4'b1111: ALU_Out = (A == B) ? 8'd1 : 8'd0; // A == B comparison
default: ALU_Out = A + B;      // Default: Addition
endcase
end
endmodule

```



K. Sowmya L^o

Signature of the Faculty